

Name \_\_\_\_\_

Date \_\_\_\_\_

Page \_\_\_\_\_

### Electrical Circuits

Fill in the following chart with information from the presentation.

<b>Slide</b>	<b>Notes</b>	<b>3-Word Summary or Illustration to Help You Remember</b>
Circuits		
Cell		
Electric Current		
Simple Circuit (2 slides)		

Circuit Diagram		
Types of Circuits		
Series Circuit		
Parallel Circuit		
Practice 1		
Practice 2		

